UPRAVLJANJE ELEKTROMOTORNIM POGONIMA Ponovljeni 2. međuispit 2009.

1. Zadani podaci su:

 $P_n = 225 \text{ kW}$

 $U_n = 2300 \text{ V}$

 $n_n = 590 \text{ r/min}$

 $f_n = 60 \text{ Hz}$


(a)

$$n_s = \frac{60f_s}{p} = \frac{60 \cdot 60}{p} = \frac{3600}{p}$$

Uvrštavanjem raznih p-ova, dobije se za p=6 sinkrona brzina $n_{\rm S}=600$ r/min. Nazivno klizanje je:

$$s_n = \frac{n_s - n_n}{n_s} = \frac{600 - 590}{600} = \frac{1}{60}$$

Bilanca snage dana je na slici ispod.

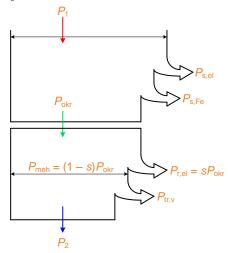

S obzirom na to da se gubici trenja i ventilacije zanemaruju, vrijedi:

$$P_2 = P_{meh} = (1 - s)P_{okr} \to P_{okr} = \frac{P_2}{1 - s}$$

Gubici u rotoru su:

$$P_{r,el} = sP_{okr}$$


Slijedi:

$$P_{r,el} = \frac{s}{1 - s} P_2$$

Motor je opterećen nazivnim momentom pa su i snaga na osovini i klizanje nazivnih vrijednosti:

$$P_{r,el} = \frac{s_n}{1 - s_n} P_n = \frac{1}{59} \cdot 225000 = 3813,6 \text{ W}$$

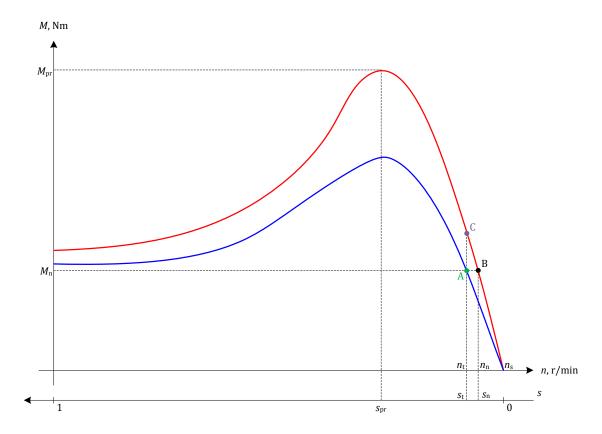(b) Momentne karakteristike dane su na slici ispod.



Točke C i B nalaze se na linearnom dijelu karakteristike pa vrijedi:

$$\frac{M_C}{S_C} = \frac{M_B}{S_B} \to \frac{M_C}{S_t} = \frac{M_n}{S_n} \to \frac{M_C}{M_n} = \frac{S_t}{S_n}$$

Klossova jednadžba za crvenu karakteristiku je:

$$\frac{M_{C}}{M_{prn}} = \frac{2}{\frac{S_{C}}{S_{prn}} + \frac{S_{prn}}{S_{C}}} = \frac{2}{\frac{S_{t}}{S_{pr}} + \frac{S_{pr}}{S_{t}}}$$

Klossova jednadžba za plavu karakteristiku je:

$$\frac{M_A}{M_{pr}} = \frac{2}{\frac{S_A}{S_{pr}} + \frac{S_{pr}}{S_A}} \rightarrow \frac{M_n}{M_{pr}} = \frac{2}{\frac{S_t}{S_{pr}} + \frac{S_{pr}}{S_t}}$$

Izjednače se Klossove jednadžbe pa slijedi:

$$\frac{M_C}{M_{prn}} = \frac{M_n}{M_{pr}} \rightarrow \frac{M_C}{M_n} = \frac{M_{prn}}{M_{pr}} = \left(\frac{U_n}{U}\right)^2$$

Boldani dio ubaci se u jednadžbu s početka zadatka:

$$\frac{s_t}{s_n} = \left(\frac{U_n}{U}\right)^2 \to s_t = s_n \left(\frac{U_n}{U}\right)^2$$

$$s_t = \frac{1}{60} \left(\frac{2300}{1950} \right)^2 = 0.0232$$

$$n_t = (1 - s_t)n_s = (1 - 0.0232) \cdot 600 = \frac{586,0881}{\text{min}}$$

Snaga na osovini je:

$$P_2 = M_n \frac{n_t \pi}{30} = \frac{30 P_n}{n_n \pi} \frac{n_t \pi}{30} = P_n \frac{n_t}{n_n} = 225000 \cdot \frac{586,0881}{590} = 223508 \text{ W}$$


Gubici u rotoru su:

$$P_{r,el} = \frac{s_t}{1 - s_t} P_2 = \frac{0,0232}{1 - 0,0232} \cdot 223508 = 5305,4 \text{ W}$$

$$i_{sa} = i_{sa} = 25\cos(75^\circ) = 6,4705 \text{ A}$$
 $i_{s\beta} = 25\sin(75^\circ) = 24,1481 \text{ A}$
 $i_{sb} = i_{sl} = 25\sin(75^\circ - 30^\circ) = 17,6777 \text{ A}$
 $i_{sc} = -25\cos(75^\circ - 60^\circ) = -24,1481 \text{ A}$
 $i_{sd} = 25\cos(75^\circ - 60^\circ) = 24,1481 \text{ A}$
 $i_{sq} = 25\sin(75^\circ - 60^\circ) = 6,4705 \text{ A}$
 $i_{sk} = 25\cos(75^\circ - 30^\circ) = 17,6777 \text{ A}$

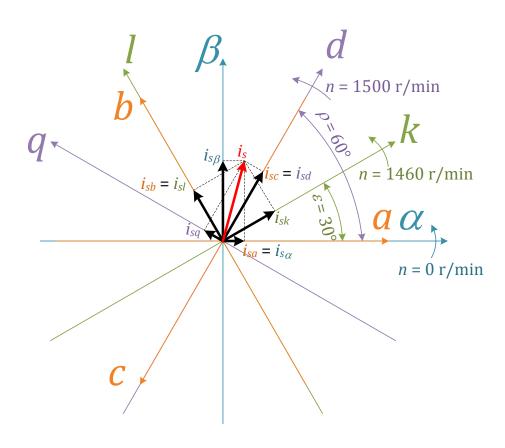(b) Kut rezultirajućeg vektora struje u (d-q) koordinatnom sustavu je:

$$\vartheta = 75^{\circ} - 60^{\circ} = 15^{\circ}$$



(c) Brzine pojedinih sustava označene su na slici iznad.

3. Zadani podaci su:

$$u_{ref} = 300 \angle 180^{\circ} \, \text{V}$$

(a) Iz kuta referentnog vektora napona slijedi da se referentni vektor napona u_{ref} nalazi između IV. i V. sektora.

$$T_s = \frac{0.2 \cdot 10^{-3}}{20\%} = \frac{0.2 \cdot 10^{-3}}{0.2} = 1 \text{ µs}$$

$$T_7 = T_8 = \frac{T_0}{2} = 0.2 \,\mu\text{s}$$

$$T_4 = T_S - T_7 - T_8 = 1 - 0.2 - 0.2 = 0.6 \,\mu\text{s}$$

(b) Za svaki kratki period T_s srednja vrijednost na izlazu iz izmjenjivača treba biti jednaka srednjoj vrijednosti referentnog vektora napona u_{ref} :

$$\frac{1}{T_{S}} \int_{0}^{T_{S}} u_{ref} dt = \frac{1}{T_{S}} \int_{0}^{T_{4}} u_{4} dt$$


$$\frac{1}{T_s} \cdot u_{ref} \cdot (T_s - 0) = \frac{1}{T_s} \cdot u_4 \cdot (T_4 - 0)$$

$$u_{ref} = u_4 \frac{T_4}{T_S}$$

$$u_{s\alpha} + ju_{s\beta} = u_{s\alpha} + j \cdot 0 = u_{s\alpha} = -\frac{2U_{DC}}{3} \frac{T_4}{T_s} \to u_{s\alpha} = -\frac{2U_{DC}}{3} \frac{T_4}{T_s} \to U_{DC} = -\frac{3u_{s\alpha}}{2} \frac{T_s}{T_4}$$

$$U_{DC} = -\frac{3 \cdot (-300)}{2} \frac{1}{0.6} = 750 \text{ V}$$

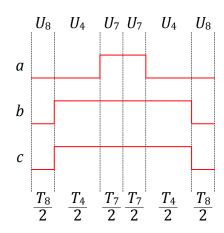(c) Valni oblici upravljačkih signala sklopki izmjenjivača prikazani su na slici ispod.



Izmjenjivač sa sklopkama prikazan je na slici ispod.

